

## Electronic Basics #14: Capacitors

### Introduction to Capacitors

A **capacitor** is a fundamental passive electronic component that stores electrical energy in an **electric field**. Unlike resistors, which dissipate energy as heat, capacitors temporarily hold charge and release it when needed. They are widely used in **power supply circuits, signal processing, timing applications, and filtering**. Capacitors come in different types, such as **ceramic, electrolytic, film, and supercapacitors**, each suited for specific applications based on capacitance value, voltage rating, and response time.

### Basic Structure: Parallel Plate Capacitor and Dielectric

A capacitor consists of **two conductive plates** separated by an **insulating material (dielectric)**. When a voltage is applied, opposite charges accumulate on each plate, creating an **electric field** between them. The capacitance (C) of a parallel plate capacitor is given by:

$$C = \epsilon A / d$$

where:

- C = capacitance (farads, F)
- $\epsilon$  = permittivity of the dielectric material
- A = surface area of the plates (m<sup>2</sup>)
- d = distance between the plates (m)

The capacitance increases with **larger plate area and smaller separation distance**.

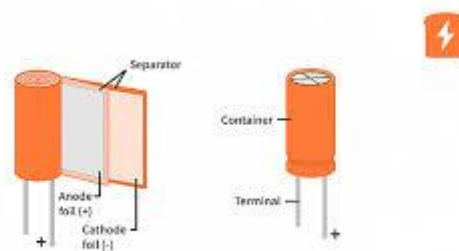


Fig14.1: Capacitor Structure

### How Does a Capacitor Work?

When connected to a **power source**, a capacitor **stores electrical charge** until it reaches the applied voltage. It does not allow continuous current flow like a resistor. Instead, it acts as a **temporary charge reservoir**, storing and releasing energy based on the circuit conditions.

- **In DC circuits**, capacitors charge up to the supply voltage and then stop conducting, effectively acting as an **open circuit**.
- **In AC circuits**, capacitors constantly charge and discharge as the voltage changes direction, allowing **AC signals to pass through** while blocking DC.

This charging and discharging behavior make capacitors useful in **energy storage, filtering, and timing applications**.

### Increasing Capacitance with Dielectric Material

The **dielectric** placed between the plates enhances capacitance by reducing the electric field strength and increasing charge storage capacity. The capacitance increases by a factor of the **dielectric constant** ( $\epsilon_r$ ), given by:

$$C = \epsilon_0 \epsilon_r \frac{A}{d}$$

where:

- $\epsilon_0$  is the permittivity of free space
- $\epsilon_r$  is the relative permittivity of the dielectric

Materials like **ceramic, mica, and plastic** are commonly used to improve capacitor efficiency.

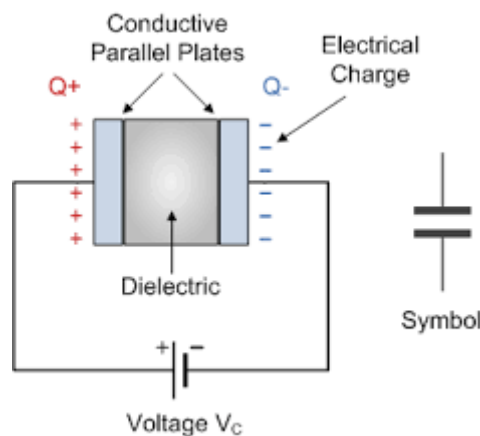


Fig14.2: Charge Storing of a Capacitor and using a di-electric medium

## Switching Operation in DC and AC Circuits

### Switching Behavior in DC Circuits

When a capacitor is connected to **DC power**, its behavior can be divided into three stages:

#### 1. Charging Phase:

- When a switch is closed, current starts flowing, and the capacitor begins to charge.
- The **voltage across the capacitor increases gradually** following the equation:

$$V_C = V_s(1 - e^{-t/RC})$$

- The **charging current is initially high** and decreases over time as the capacitor approaches full charge.

## 2. Fully Charged State (Steady-State):

- After a long time ( $t \gg RC$ ), the capacitor is fully charged, and current stops flowing.
- The capacitor now acts as an **open circuit, blocking further DC current**.

## 3. Discharging Phase:

- When the power source is disconnected and the capacitor is connected to a load, it **discharges**, releasing stored energy.
- The voltage across the capacitor decreases exponentially:

$$V_C = V_s e^{-t/RC}$$

- This property is used in **memory storage, power backup circuits, and pulsed power applications**.

## Switching Behavior in AC Circuits

In **AC circuits**, capacitors continuously charge and discharge as the voltage changes direction. Unlike DC, where a capacitor eventually blocks current, in an AC circuit, the capacitor **allows current to flow by constantly responding to voltage variations**.

### 1. Continuous Charging and Discharging:

- As AC voltage **increases**, the capacitor stores charge.
- When AC voltage **reverses polarity**, the capacitor discharges and recharges in the opposite direction.
- This process **allows AC signals to pass through**, making capacitors useful for **coupling and filtering applications**.

### 2. Frequency Dependence:

- At **higher frequencies**, a capacitor charges and discharges faster, allowing more current to pass.
- At **lower frequencies**, the capacitor charges and discharges more slowly, restricting current flow.
- This property is used in **frequency-dependent circuits like filters and oscillators**.

### 3. Phase Shift in AC Circuits:

- In a **purely capacitive circuit**, the **current leads the voltage by 90°**.
- This means the **current reaches its peak before the voltage does**, which is important in **power factor correction and reactive power management**.

## Capacitive Reactance and Formula

The **opposition** a capacitor offers to AC is called **capacitive reactance ( $X_C$ )**, given by:

$$X_C = 1 / 2\pi fC$$

where:

- $X_C$  = capacitive reactance (ohms,  $\Omega$ )
- $f$  = frequency (Hz)
- $C$  = capacitance (farads)

As frequency increases,  $X_C$  **decreases**, meaning capacitors allow higher-frequency signals to pass more easily. This makes them useful in **high-pass filters, signal processing, and AC coupling applications**.

### Applications of Capacitors

- **Energy Storage:** Stores energy in flash cameras, UPS systems, and power backup circuits.
- **Signal Filtering:** Removes noise and unwanted frequencies in communication circuits.
- **AC-DC Conversion:** Smooths voltage output in rectifier circuits.
- **Timing Circuits:** Used in clocks, pulse generators, and oscillators.
- **Motor Starters:** Provides phase shift for efficient induction motor operation.
- **Power Factor Correction:** Improves efficiency in AC power systems by compensating for inductive loads.