

## Electronic Basics #16: Resistors

### Introduction to Resistors

A **resistor** is a fundamental passive electronic component that opposes the flow of electric current. It is widely used in circuits for **voltage division, current limiting, signal conditioning, and power dissipation**. Resistors come in various types, materials, and values, making them essential in almost all electronic and electrical applications. The resistance of a resistor is measured in **ohms ( $\Omega$ )** and follows **Ohm's Law**, which states:

$$V=IR$$

where:

- V = voltage across the resistor (volts)
- I = current flowing through the resistor (amperes)
- R = resistance (ohms)



Fig16.1: Resistor

### Resistor Color Code Chart

Resistor color coding is a standard method to indicate **resistance values** using **colored bands** printed on the resistor body. This system follows the **Electronic Industries Association (EIA) standard** and is commonly used for through-hole resistors.

### Understanding the Color Code

A standard **4-band resistor** has:

**First Band** – First significant digit

**Second Band** – Second significant digit

**Multiplier** – Power of ten ( $10^n$ )

**Tolerance** – Accuracy of the resistor

A **5-band resistor** includes an extra **third significant digit**, improving precision.

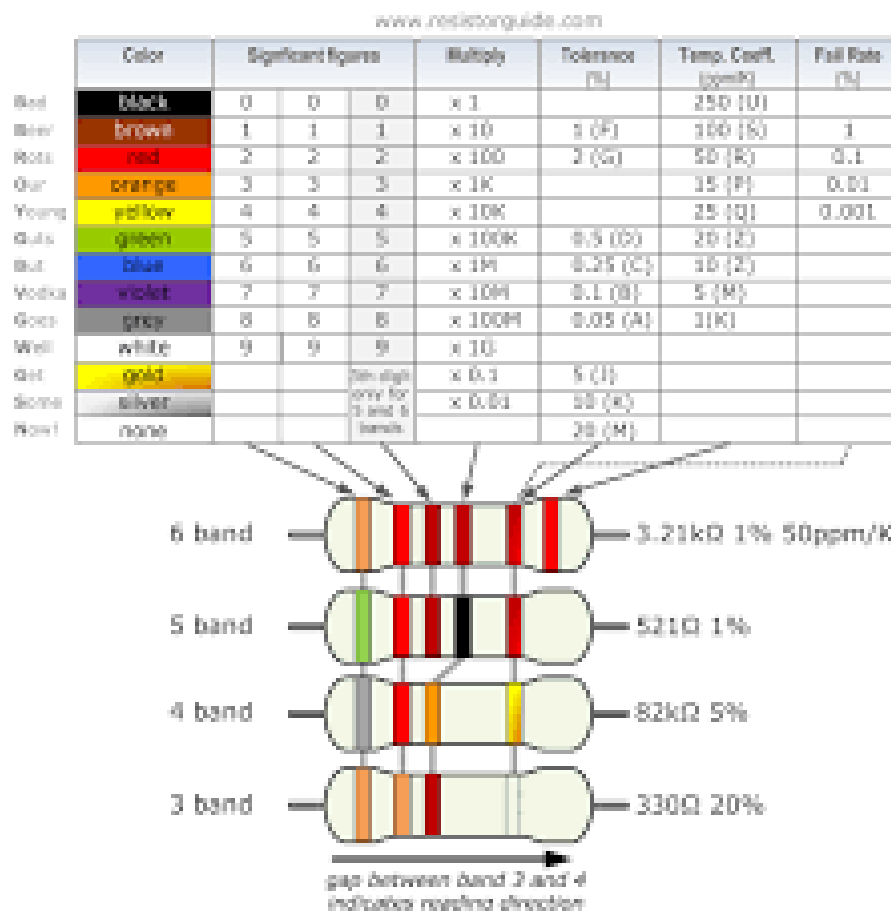


Fig16.2: Resistor Color Code Chart

## Types of Resistors

### Fixed Resistors

Fixed resistors have a **constant resistance value** that does not change under normal conditions. Common types include:

- **Carbon Composition Resistors** – Cheap but less precise.
- **Metal Film Resistors** – More accurate and stable.
- **Wirewound Resistors** – High power handling capability.

### Variable Resistors (Potentiometers & Rheostats)

These resistors allow for **adjustable resistance** by sliding or rotating a contact.

- **Potentiometers** – Used for **volume control** in audio circuits.
- **Rheostats** – Used for **current control** in motors and lighting.

### Special Purpose Resistors

- **Thermistors** – Temperature-dependent resistors (NTC/PTC).
- **LDR (Light Dependent Resistors)** – Changes resistance based on light intensity.

- **Shunt Resistors** – Low-value resistors used for **current measurement**.

### How Resistors Work

Resistors work by **converting electrical energy into heat** as they oppose current flow. The amount of heat generated is given by **Joule's Law**:

$$P = I^2 R$$

where:

- $P$  = power dissipated (watts)
- $I$  = current (amperes)
- $R$  = resistance (ohms)

In a **series circuit**, resistors **add up**:

$$R_{\text{total}} = R_1 + R_2 + R_3 + \dots$$

In a **parallel circuit**, resistances combine as:

$$\frac{1}{R_{\text{total}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

### Creating a Voltage Divider

A **voltage divider** is a simple circuit that **splits a voltage into a lower desired value** using **two resistors in series**. It is widely used in sensor interfacing, reference voltage generation, and signal scaling. The output voltage is given by:

$$V_{\text{out}} = V_{\text{in}} \times \frac{R_2}{R_1 + R_2}$$

where:

- $V_{\text{in}}$  is the input voltage,
- $V_{\text{out}}$  is the reduced output voltage,
- $R_1$  and  $R_2$  are the resistors in series.

For example, to step down 5V to 3.3V, choosing  $R_1 = 1\text{k}\Omega$  and  $R_2 = 2\text{k}\Omega$  will give the desired output voltage. This method is commonly used in microcontroller ADC inputs, biasing circuits, and power supply adjustments.

### Resistors in Current Limiting Applications

In circuits, resistors **protect components** by limiting excessive current. For example, in an LED circuit, a **series resistor** prevents the LED from burning out. The required resistance is calculated as:

$$R = \frac{V_{\text{source}} - V_{\text{LED}}}{I_{\text{LED}}}$$

where  $V_{\text{LED}}$  is the LED forward voltage and  $I_{\text{LED}}$  is the desired current.

## Resistors in Signal Conditioning

Resistors are used in **pull-up and pull-down configurations** in digital circuits to maintain defined logic levels.

- **Pull-up resistor** – Connects a pin to **Vcc** to keep it HIGH.
- **Pull-down resistor** – Connects a pin to **GND** to keep it LOW.

These are crucial in **microcontroller inputs, communication protocols, and sensor interfaces**.

## Using Resistors in Wheatstone Bridge Circuits

A **Wheatstone bridge** uses **four resistors** in a balanced configuration to **precisely measure unknown resistance**. The output voltage is given by:

$$V_{out} = V_{in} \times \frac{R_2 R_1 + R_2 - R_4 R_3 + R_4}{R_1 + R_2 + R_3 + R_4}$$

This is commonly used in **strain gauges, temperature sensors, and precision measurement instruments**.

## Power Rating of Resistors

Resistors have a **power rating** (in watts) that defines how much power they can safely dissipate without overheating. Common power ratings include **1/4W, 1/2W, 1W, and 5W**. Choosing a resistor with an appropriate power rating prevents **overheating and circuit failure**.

$$P = VI = I^2 R = \frac{V^2}{R}$$

## Applications of Resistors

- **Voltage Regulation** – Used in **voltage dividers and regulators**.
- **Current Limiting** – Protects LEDs, transistors, and ICs.
- **Signal Processing** – Forms **RC filters in audio and communication circuits**.
- **Temperature Sensing** – Thermistors for environmental monitoring.
- **Precision Measurements** – Used in **Wheatstone bridge circuits**.

## Resistors in AC Circuits

In **AC circuits**, resistors behave similarly to how they do in DC circuits, following **Ohm's Law ( $V=IR$ )**. However, unlike inductors and capacitors, resistors do **not introduce phase shift** between voltage and current. The current and voltage remain **in phase**, meaning their peaks and zero-crossings occur simultaneously.

The **power dissipation** in an AC resistor is given by:

$$P = V_{rms} I_{rms} \cos \theta_p$$

Since the phase angle  $\theta = 0^\circ$  is **always 1**, meaning all power is converted into heat.

### Why Does Current Increase When Frequency Increases?

For a **pure resistor**, the current does **not depend on frequency** because resistance is a fixed property. However, in **practical circuits**, resistors often have **small parasitic inductance and capacitance**, which affect the current at higher frequencies.

- **Parasitic Inductance:** At very high frequencies, even a straight resistor wire behaves like an inductor, slightly opposing the current.
- **Parasitic Capacitance:** Some resistors exhibit small **capacitive effects**, allowing **more current to pass at high frequencies**, reducing overall impedance.

In circuits where resistors are combined with **capacitors or inductors**, **reactance (XX)** plays a role, and the total impedance changes with frequency, affecting current flow.

Resistors are **fundamental** components in electronics, playing a crucial role in **controlling voltage, limiting current, signal processing, and power dissipation**. Their **versatility, reliability, and ease of use** make them indispensable in all types of electrical and electronic systems.