

Electronic Basics #10: Digital to Analog Converter (DAC):

Introduction

A **Digital-to-Analog Converter (DAC)** is a device that converts digital signals (binary data) into analog signals (continuous voltage or current). One of the most efficient and widely used methods for DAC implementation is the **R-2R Ladder DAC**, which offers precision with a simple resistor network.

Digital and Analog Signals

- **Digital Signal:** A discrete signal represented by binary values (0s and 1s), used in computers and microcontrollers.
- **Analog Signal:** A continuous signal that varies over time, used in real-world applications like audio, video, and sensor outputs.

R-2R Ladder DAC Method

The **R-2R Ladder DAC** is a resistor-based network that converts digital input into an analog output. It consists of only two resistor values: **R** and **2R**, arranged in a repetitive pattern. This ladder-like structure acts as a **voltage divider**, converting each digital bit into a corresponding weighted voltage contribution.

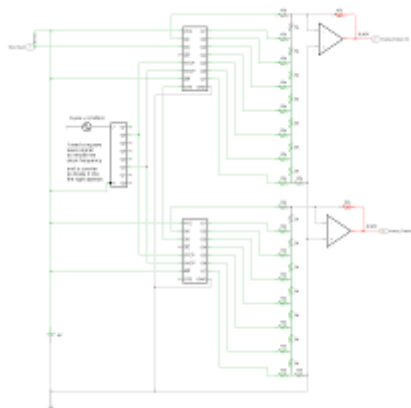


Fig10.1: R2R Lader Methode Diagram

Principle and 8-bit System

The output voltage (V_{out}) is calculated using the weighted sum formula:

$$V_{out} = V_{ref} \times (D_7 + D_6 + D_5 + \dots + D_0 \cdot 2^{-7})$$

For an **8-bit system** ($2^8 = 256$ levels), the digital input ranges from **00000000 (0V)** to **11111111 (close to V_{ref})**, providing 256 discrete voltage levels. The **Most Significant Bit (MSB)** has the highest weight, and the **Least Significant Bit (LSB)** has the lowest contribution.

How to Use the R-2R Ladder DAC?

1. **Connect digital inputs (D0–D7) to a microcontroller or binary signal source.**
2. **Apply a reference voltage (V_{ref}).**
3. **Use an operational amplifier (op-amp) for buffering and smooth output.**
4. **The resistor network converts the binary input into an equivalent analog voltage.**

Applications of R-2R DAC

- **Audio Signal Processing** (music players, sound cards).
- **Waveform Generation** (oscilloscopes, function generators).
- **Microcontroller-based Analog Output** (PWM-to-analog conversion).
- **Communication Systems** (modulation, signal transmission).

The **R-2R Ladder DAC** is preferred in digital systems due to its simplicity, precision, and scalability, making it a key component in modern electronic circuits.