

VIDEO#26: Electronic Basics #26: 555 Timer IC

The 555 Timer IC

Introduction to the 555 Timer IC

The 555 Timer IC is one of the most widely used integrated circuits in electronics. It is commonly used for generating precise time delays, oscillation, and pulse width modulation. The IC operates by attaching external components to configure it in different modes, allowing it to perform various functions in electronic circuits.

Internal Structure of the 555 Timer IC

The 555 Timer consists of several internal components that contribute to its functionality. It has eight pins, each serving a specific purpose. A series of three **5-kiloohm resistors** between pin 1 (GND) and pin 8 (VCC) form a voltage divider. This resistor network plays a crucial role in setting the reference voltages for internal comparators.

Pin Configuration:

1. **Pin 1 (GND):** Ground connection.
2. **Pin 2 (Trigger):** Connected to the negative input of a comparator, which determines when the timer starts.
3. **Pin 3 (Output):** The main output pin, which delivers a high or low signal.
4. **Pin 4 (Reset):** Used to reset the flip-flop when connected to ground.
5. **Pin 5 (Control Voltage):** Allows modification of the reference voltage for comparators.
6. **Pin 6 (Threshold):** Connected to the positive input of a comparator, used to determine when to reset the timer.
7. **Pin 7 (Discharge):** Connected to a transistor that discharges an external capacitor.

8. **Pin 8 (VCC):** The power supply voltage (usually 5V to 15V).

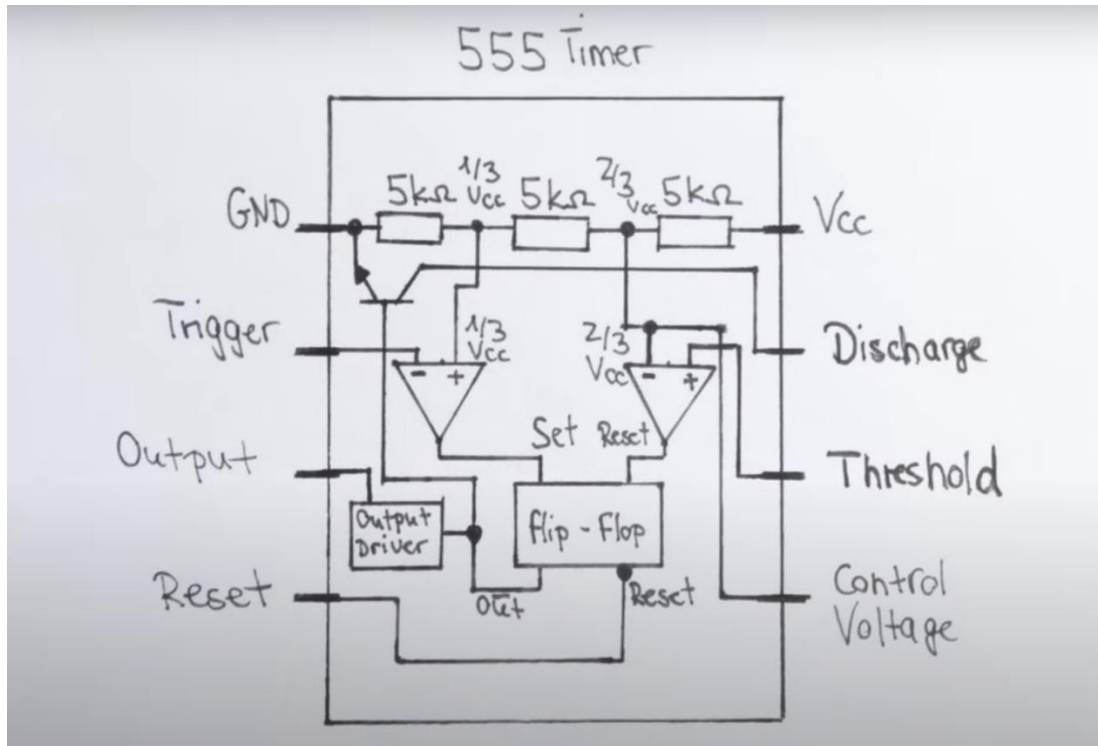


Fig: Structure of 555 Timer

Internal Working of the 555 Timer IC

The IC includes:

- **Voltage Divider:** Formed by three 5kΩ resistors, setting reference points at $\frac{1}{3}$ and $\frac{2}{3}$ of the supply voltage.
- **Comparators:** Two comparators compare external voltage inputs with the reference voltages.
- **Flip-Flop:** Stores and toggles states based on comparator outputs.
- **Output Driver:** Provides the final output signal.
- **Discharge Transistor:** Discharges external capacitors when necessary.

The comparators and flip-flop together determine the output state based on external signals applied to the trigger and threshold pins.

Operating Modes of the 555 Timer

The 555 Timer can be configured in three basic modes: **Monostable**, **Bistable**, and **Astable**.

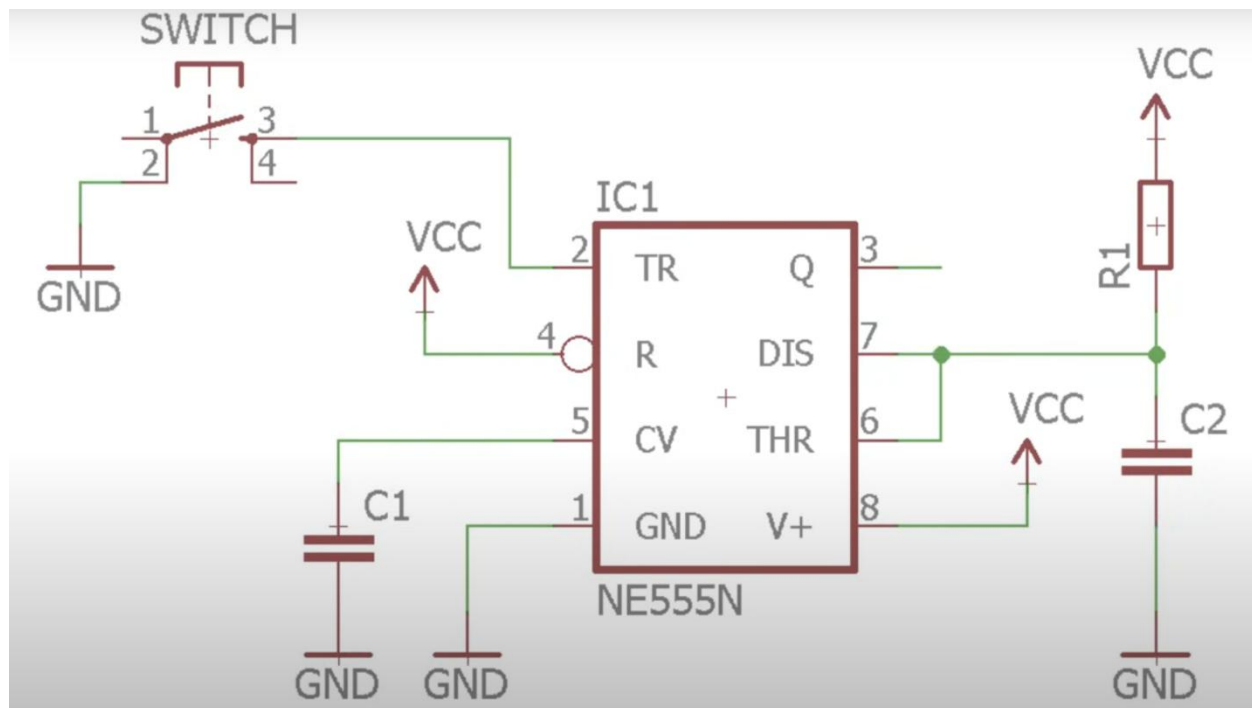


Fig: ckt for monostable Multivibrator

1. Monostable Multivibrator

- Also known as a **one-shot pulse generator**.
- The circuit remains in a stable low state until triggered.
- When triggered (by pulling Pin 2 to ground), the capacitor starts charging.
- Once the capacitor voltage reaches $\frac{2}{3} V_{CC}$, the output returns to low.
- The duration of the high pulse is determined by the resistor-capacitor (RC) combination.
- **Application:** Used in **delay circuits** such as notification lights.

2. Bistable Multivibrator

- Has **two stable states** (high and low).
- No capacitors are required.
- Triggering Pin 2 (low) **sets the output high**.
- Triggering Pin 6 (low) **resets the output to low**.

- **Application:** Used in **toggle switches** for turning LEDs or other devices ON/OFF.

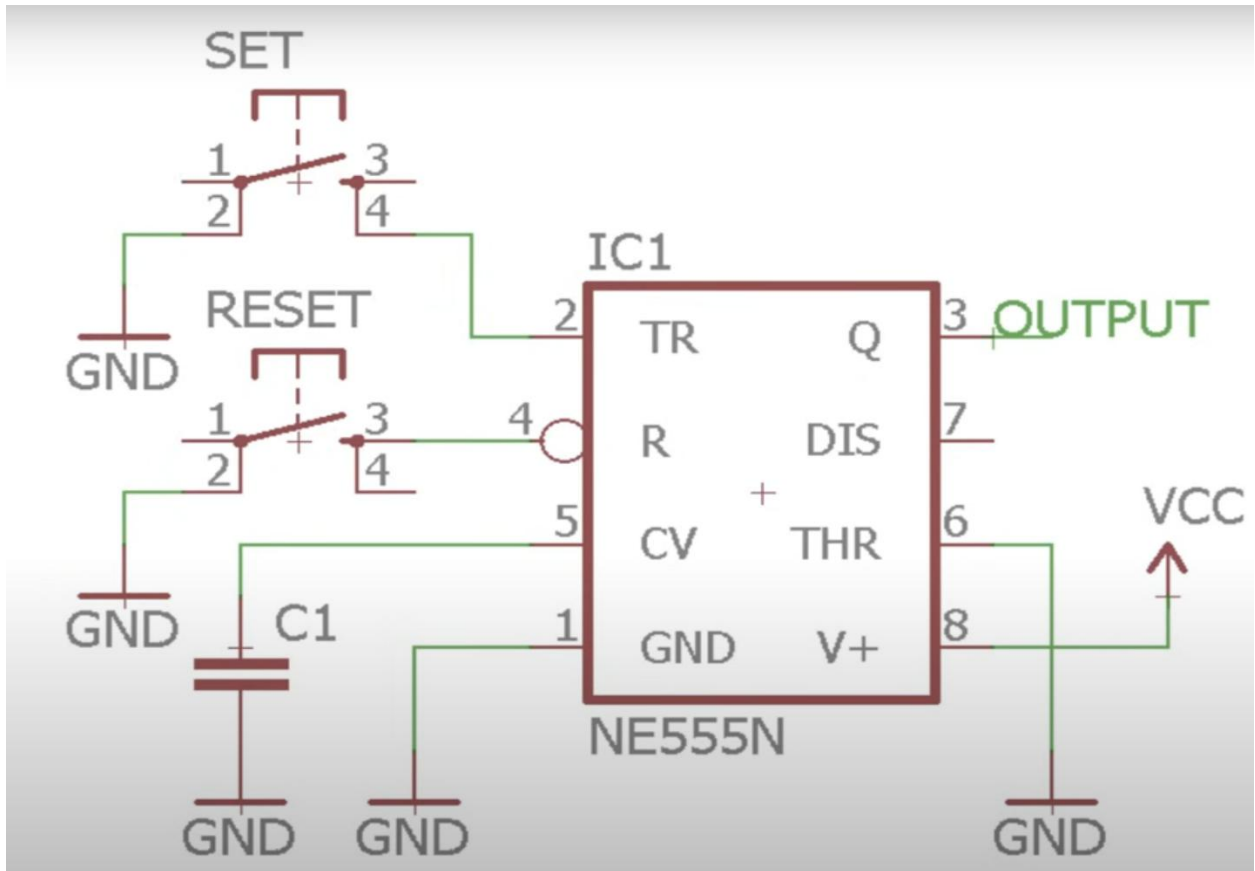


Fig: ckt for Bistable Multivibrator

3. Astable Multivibrator

- Operates as an **oscillator**, generating a continuous **square wave** output.
- The capacitor charges through **two resistors (R1 & R2)** and discharges only through **R2**.
- The **on-time** of the output signal depends on both R1 and R2, while the **off-time** is determined only by R2.
- **Modification for PWM:** Adding **diodes** allows separate control of charge and discharge times.
- **Application:** Used in **timing circuits, clock generation, and waveform generation**.

Improving the 555 Timer Performance

The standard **NE555** timer uses bipolar junction transistors (BJTs), which introduce voltage drops and limit performance. A better alternative is the **CMOS 555 Timer (TLC555)**:

- **Advantages:**
 - Can achieve an **output voltage close to VCC**.
 - **Consumes less power**.
 - **Operates at higher frequencies**.
 - Works with **lower supply voltages**.
- **Disadvantage:** Cannot supply as much current as the standard **NE555**.

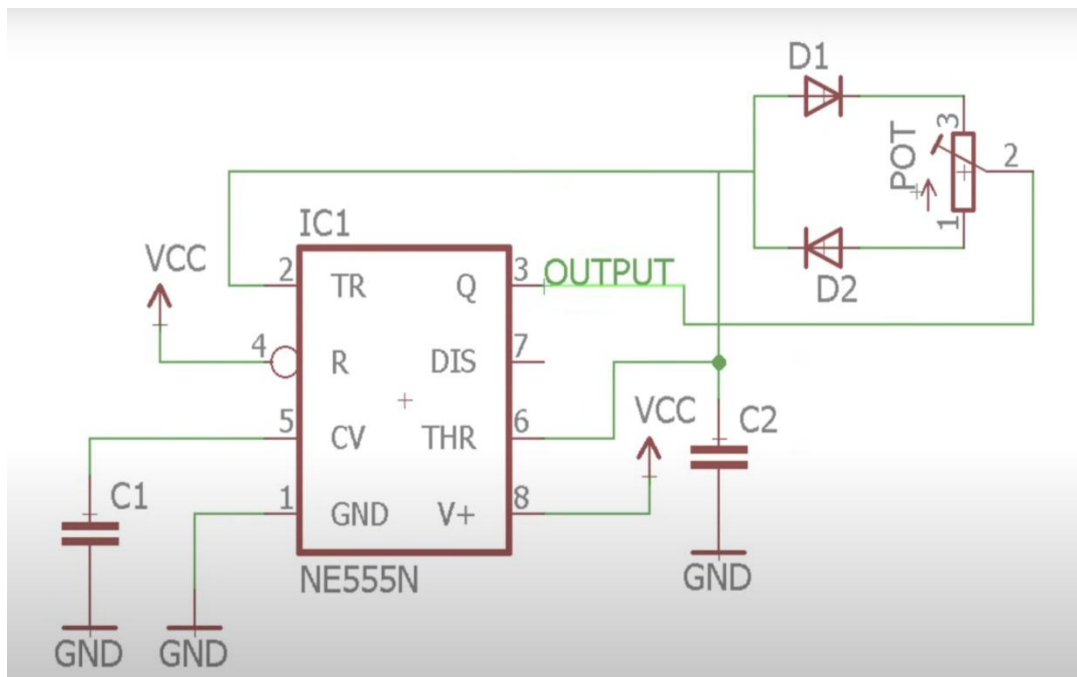


Fig: CMOS 555 timer configuration

Pulse Width Modulation (PWM) using the 555 Timer

- PWM signals can be generated using an **Astable 555 Timer**.
- Adjusting **charging and discharging resistances separately** allows control of the duty cycle.

- **Replacing resistors with diodes and a potentiometer** helps fine-tune the charging and discharging time independently.
- **Application:** Used in **motor speed control, dimming LEDs, and power regulation circuits.**

The **555 Timer IC** is a versatile component with widespread applications in electronics. By configuring external resistors and capacitors, it can function as a **monostable, bistable, or astable multivibrator**, allowing it to serve as a delay timer, flip-flop switch, or oscillator. The introduction of **CMOS variants** further enhances its efficiency for specific applications like PWM control. Understanding its internal working and practical configurations is essential for designing robust electronic circuits. The 555 Timer is built using comparators, flip-flops, and transistors. It has **three main operating modes**: Monostable, Bistable, and Astable. The **CMOS version (TLC555)** offers better efficiency than the **NE555**. Used in **timing, pulse generation, frequency modulation, and PWM control**. **Common applications** include LED control, motor speed regulation, waveform .